

W5300 IP 3D Camera over Single Pair Ethernet MCU and Power Supply Part

19th August 2023

Jaroslav Juda

jarojuda@gmail.com

<https://github.com/jarojuda>

MCU.....	1
Power Supply.....	1
Fig. 1. MCU schematics.....	2
Fig. 2. Power supply schematics.....	3

MCU

The [STM32U575ZI](#) was chosen for its low power consumption and high computing power.

Supply voltage 3.3V.

16MHz external quartz clock.

Interfaces used:

- I2C to control ToF sensors and camera
- SPI to emulate MDIO for ADIN1100
- USB for diagnostics
- DCMI for the OV2640 camera module
- FMC for the W5300 Internet coprocessor

Power Supply

The device can be powered from three sources:

- Locally from a 24V power supply,
- Remotely via Power over Data Line
- Via USB with 5V voltage

PoDL and 24V power goes through the [TPS26400](#) protection chip which has the following thresholds set: 18V undervoltage, 30V overvoltage and 0.2A current limit. An isolated DC/DC converter provides an output voltage of 3.3 V.

Power from USB goes through the [LDL112PV3R](#) LDO with reverse current protection.

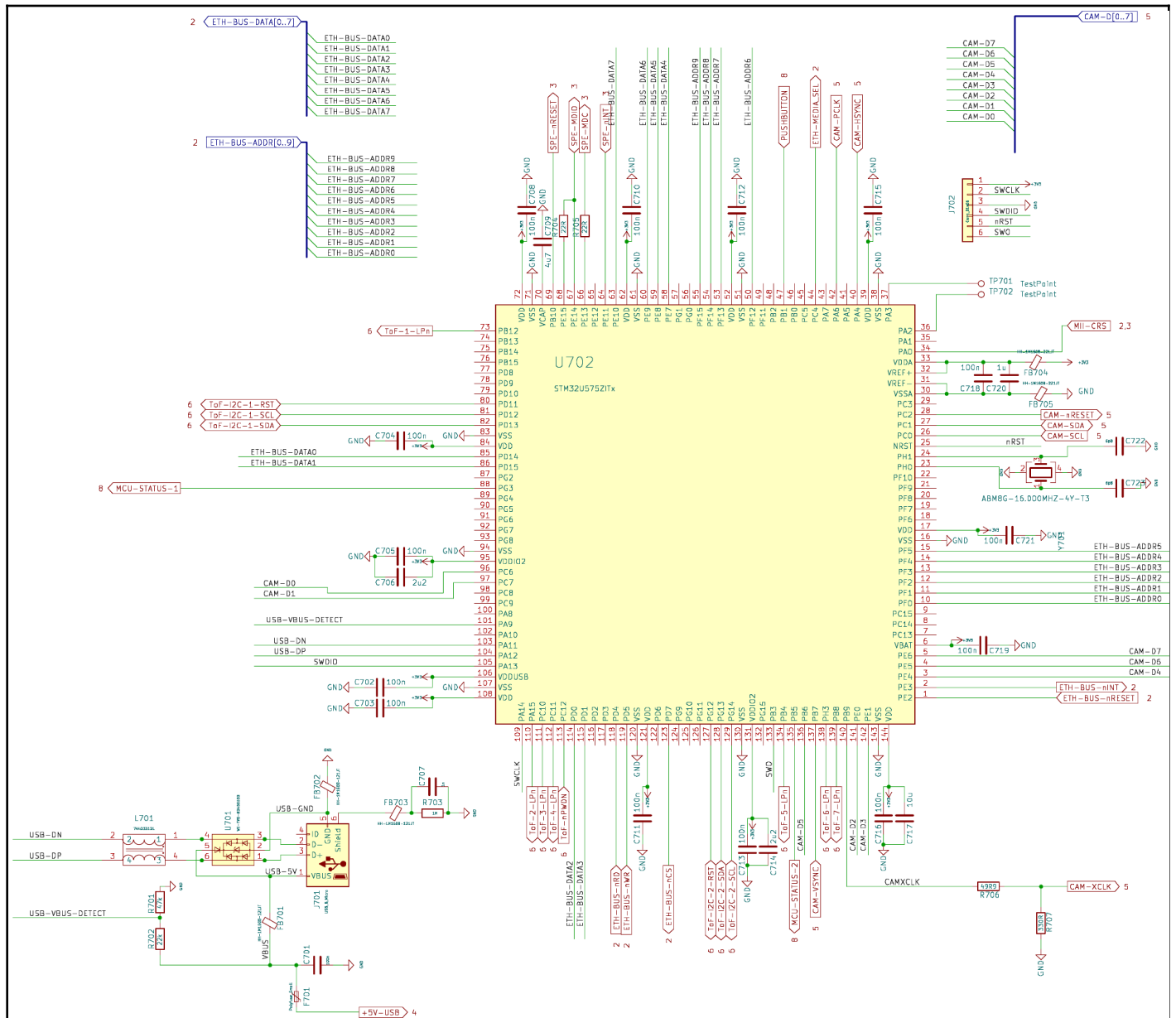


Fig. 1. MCU schematics

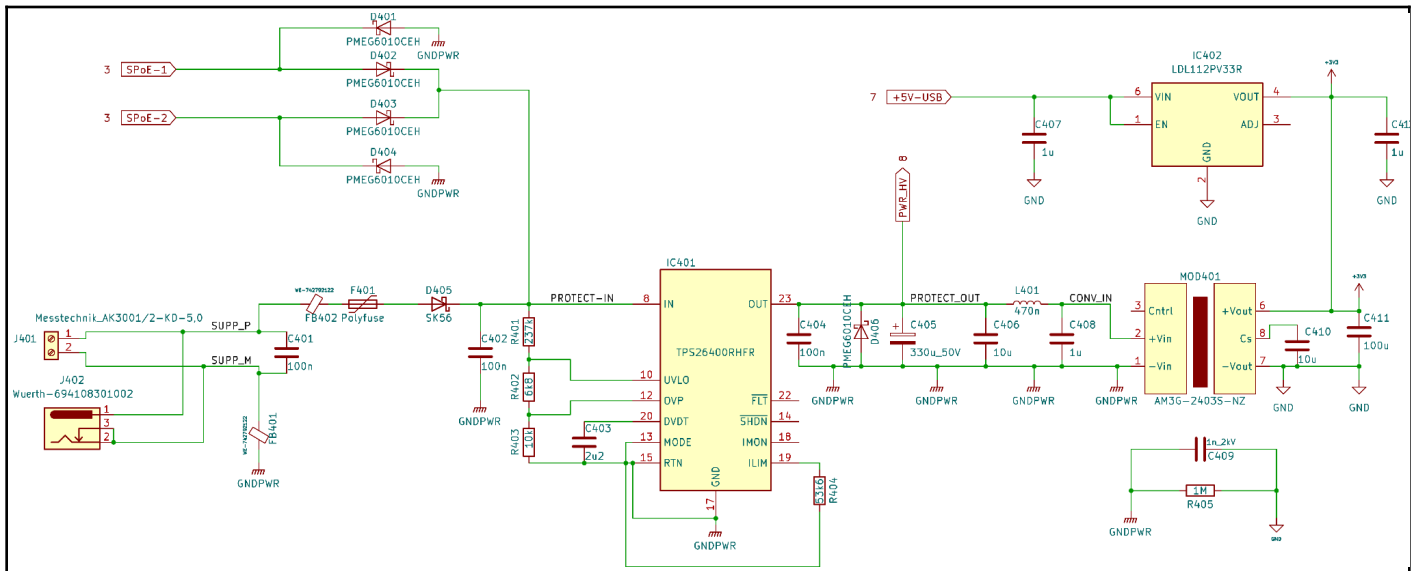


Fig. 2. Power supply schematics